



上海科技大学
ShanghaiTech University

EE171 Project: Single-phase SPWM Modulation Inverter

梁家伟

2019.06.11

Contents



- Design an inverter using bipolar modulation.
- Design an inverter using unipolar modulation.
- Design an inverter to eliminate 5th and 7th order harmonics of U_o and present your results.
- Have a brief discussion or comparison about the simulation results.

Parameter

Parameter	Value
DC input U_d	400V
Fundamental wave RMS $U_{o1,rms}$	220V
Modulation wave Frequency f_r	50Hz
Carrier wave Frequency f_c	2000Hz
Amplitude Modulation Index	$m_a = \frac{A_r}{A_c} = \frac{U_{o1}}{U_d} \approx 0.778$
Frequency Modulation Index	$m_f = \frac{f_c}{f_r} = \frac{2000}{50} = 40$


Bipolar PWM Simulation Model

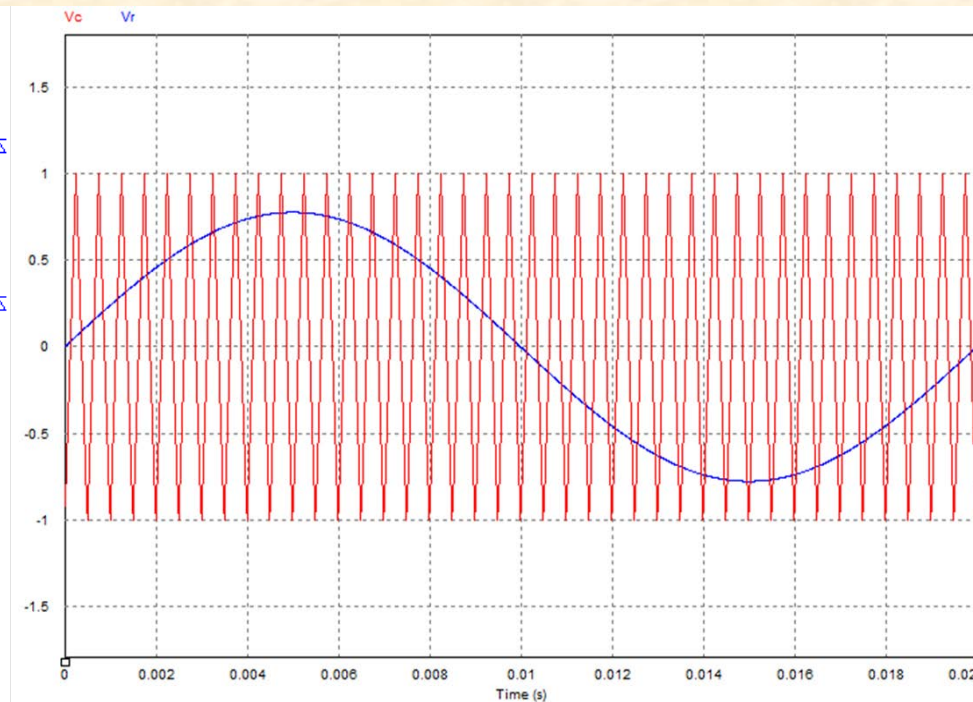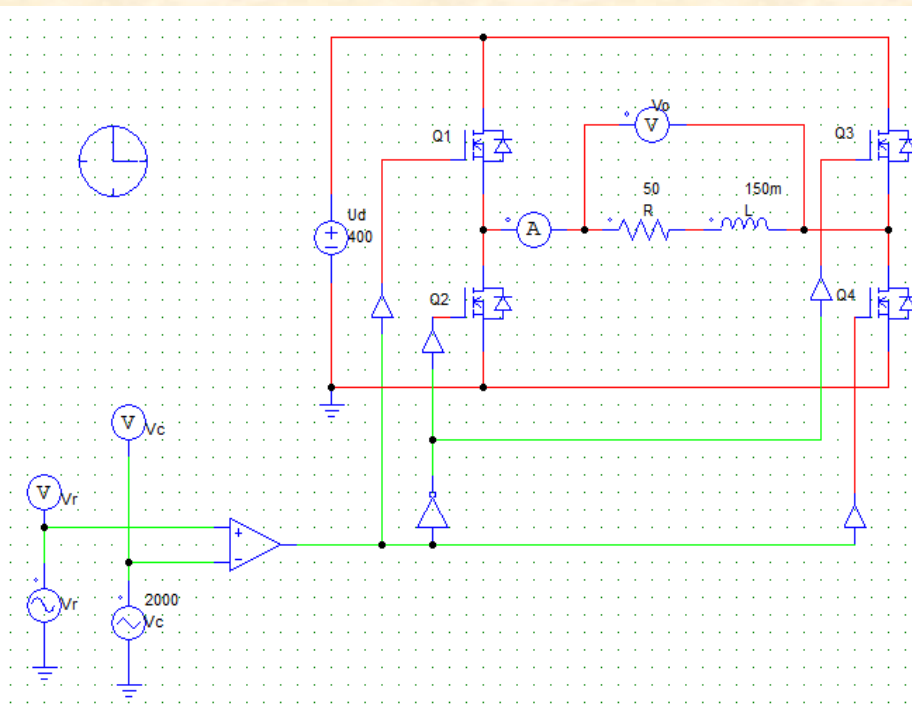- $V_r > V_c$, turn on Q_1, Q_4 and turn off Q_2, Q_3 .
- $V_r < V_c$, turn on Q_2, Q_3 and turn off Q_1, Q_4 .




Bipolar PWM Simulation Results

- Output PWM wave

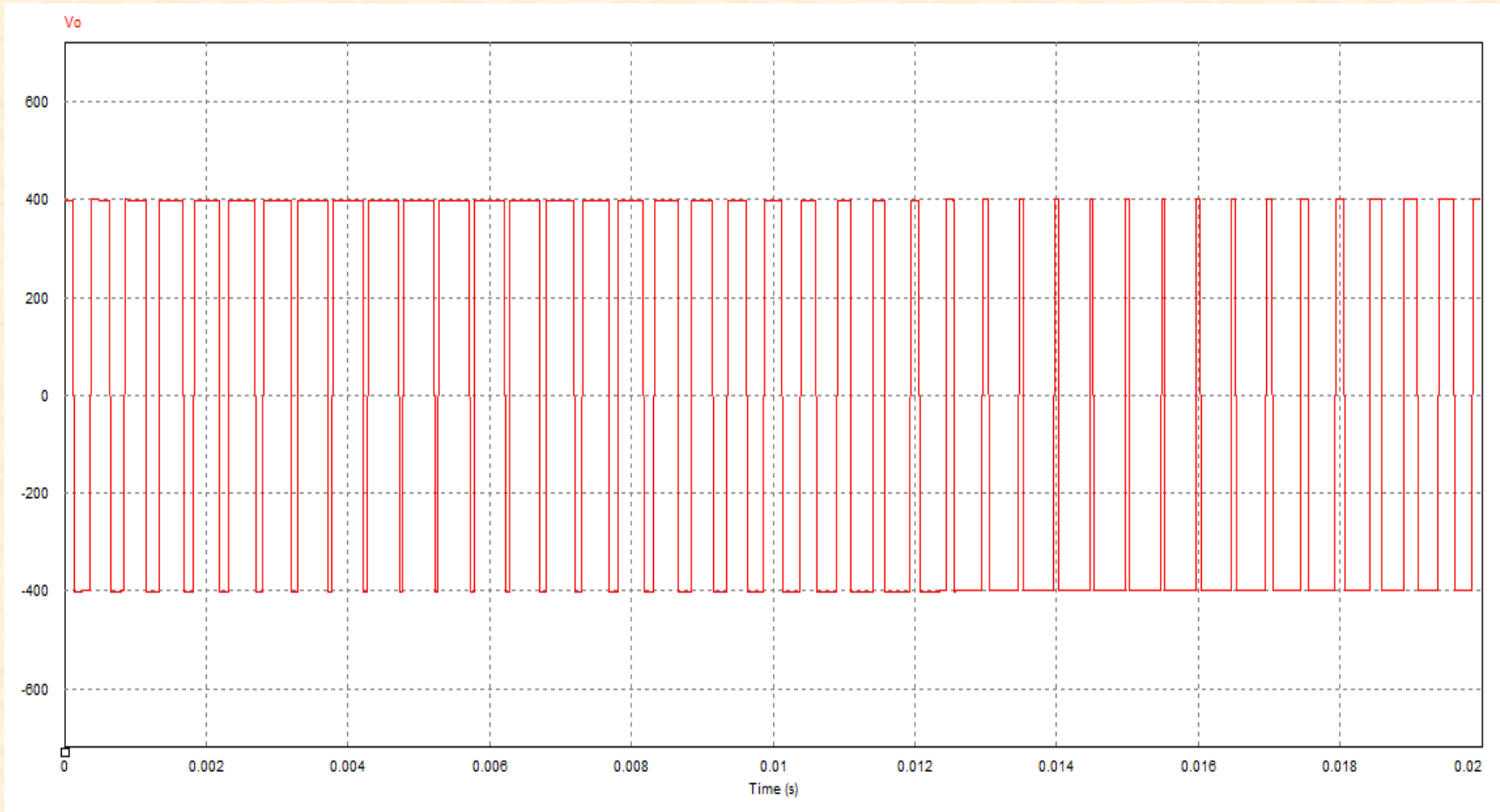

Bipolar PWM Simulation Results


- FFT analysis

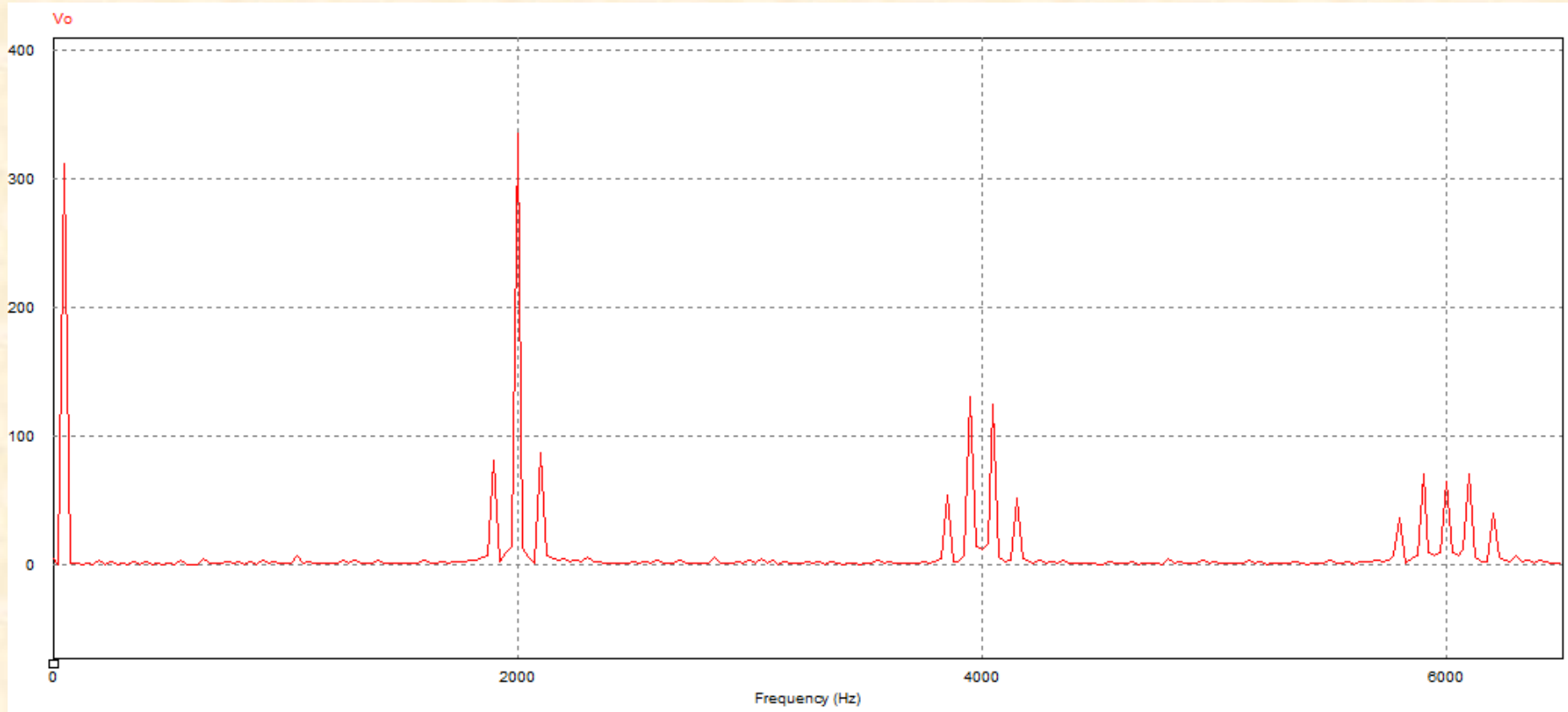

- $U_{o1} = 303V$, $RMS = \frac{303}{\sqrt{2}} \approx 214.25V$

Bipolar PWM Simulation Results


- Output current I_o

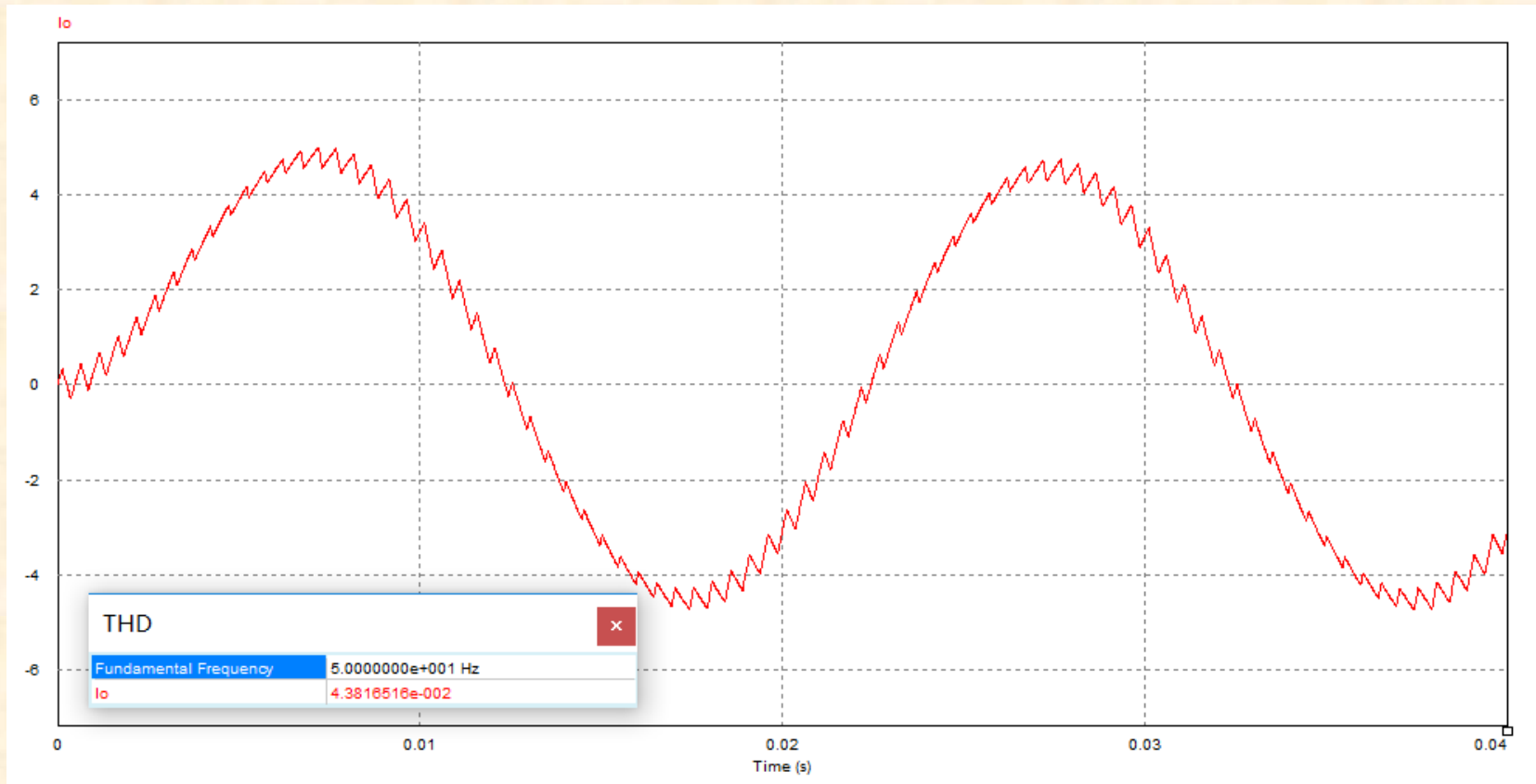

$$THD = 4.38\%$$


Unipolar PWM Simulation Model

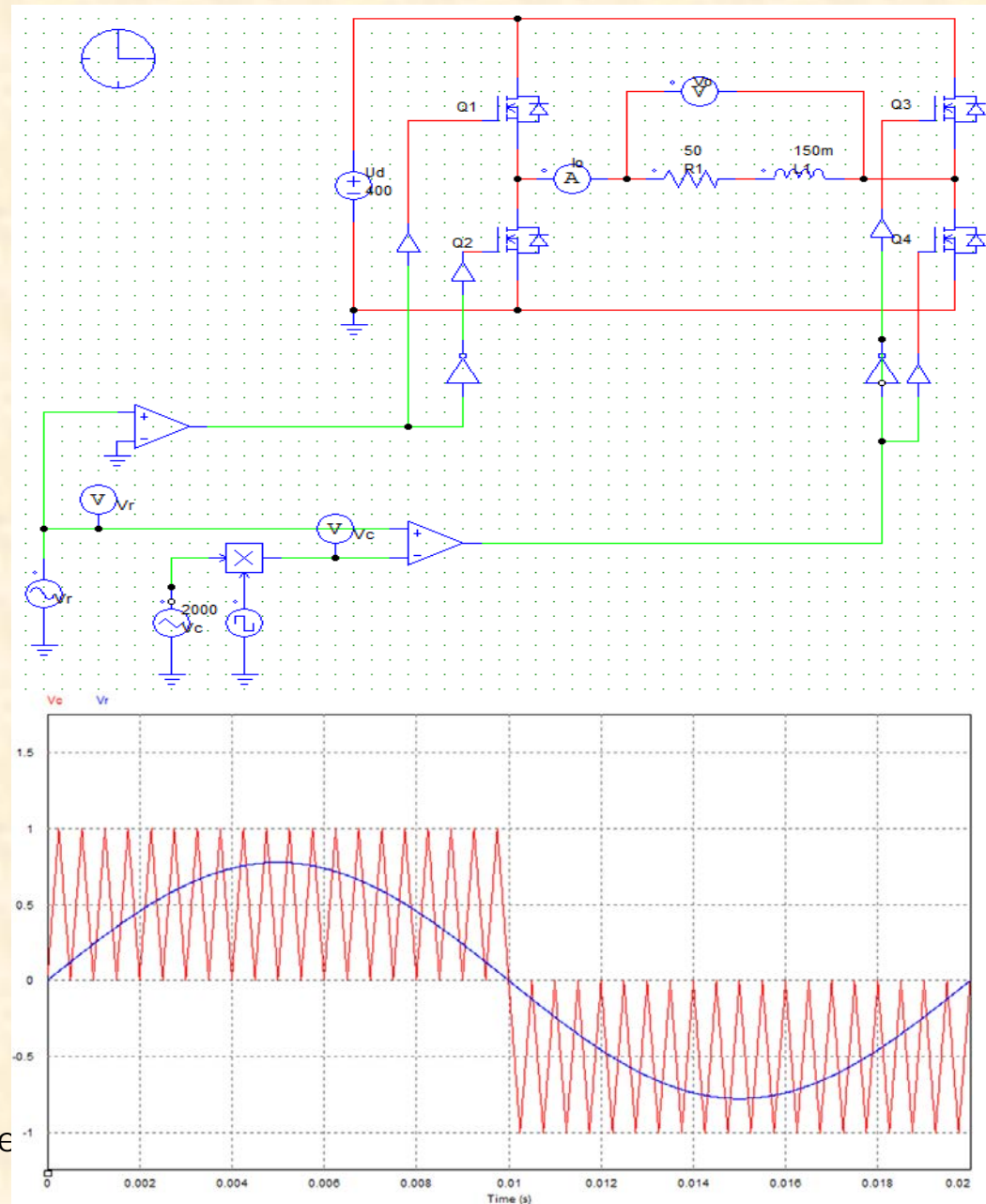- $V_r > 0$, keep Q_1 on and Q_2 off.
 - When $V_r > V_c$, turn on Q_4 and turn off Q_3 , $U_0 = U_d$.
 - When $V_r < V_c$, turn on Q_3 and turn off Q_4 , $U_0 = 0$.
- $V_r < 0$, keep Q_2 on and Q_1 off.
 - When $V_r > V_c$, turn on Q_4 and turn off Q_3 , $U_0 = 0$.
 - When $V_r < V_c$, turn on Q_3 and turn off Q_4 , $U_0 = U_d$.




Unipolar PWM Simulation Results

- Output PWM wave

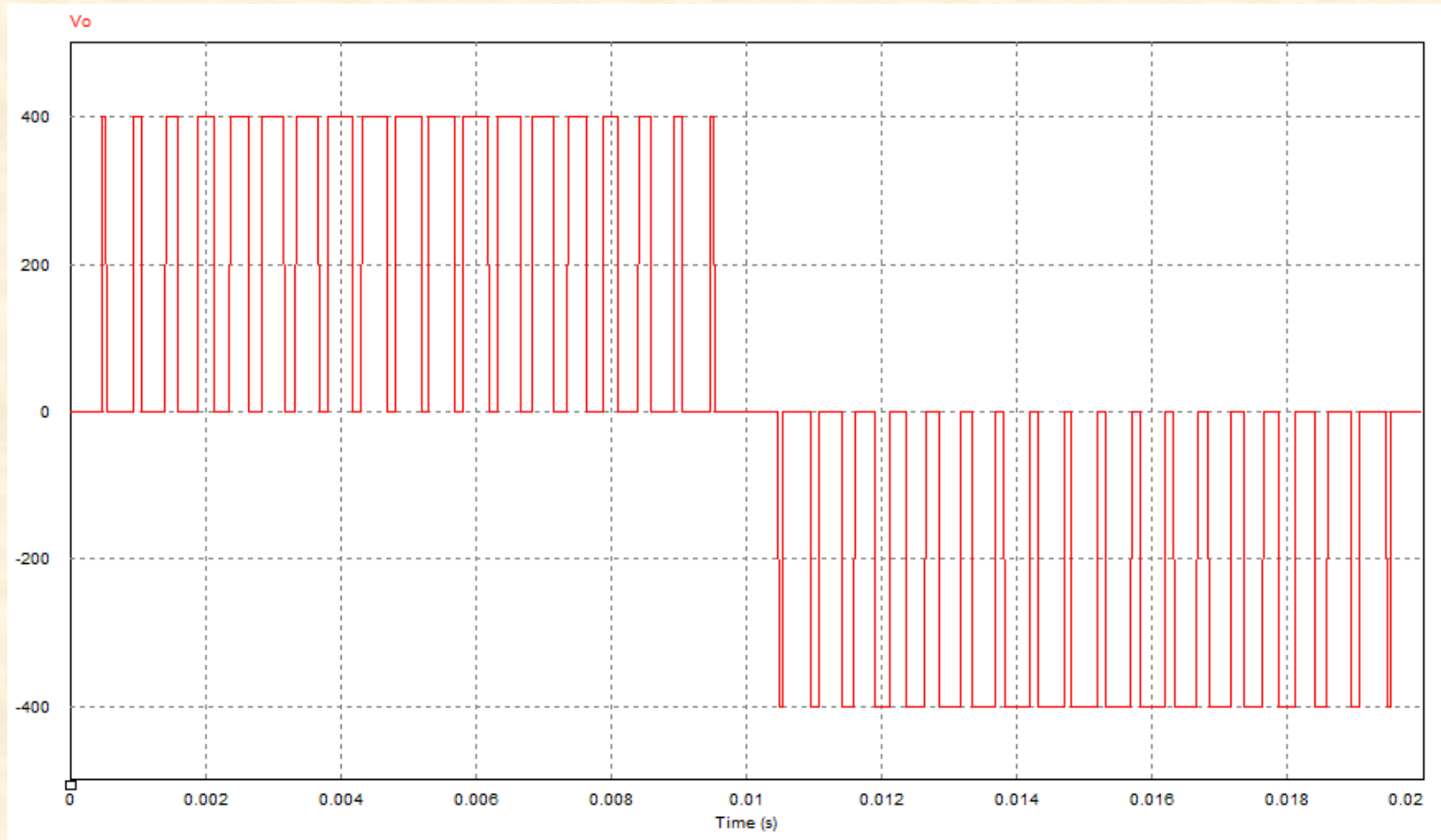

Unipolar PWM Simulation Results


- FFT analysis

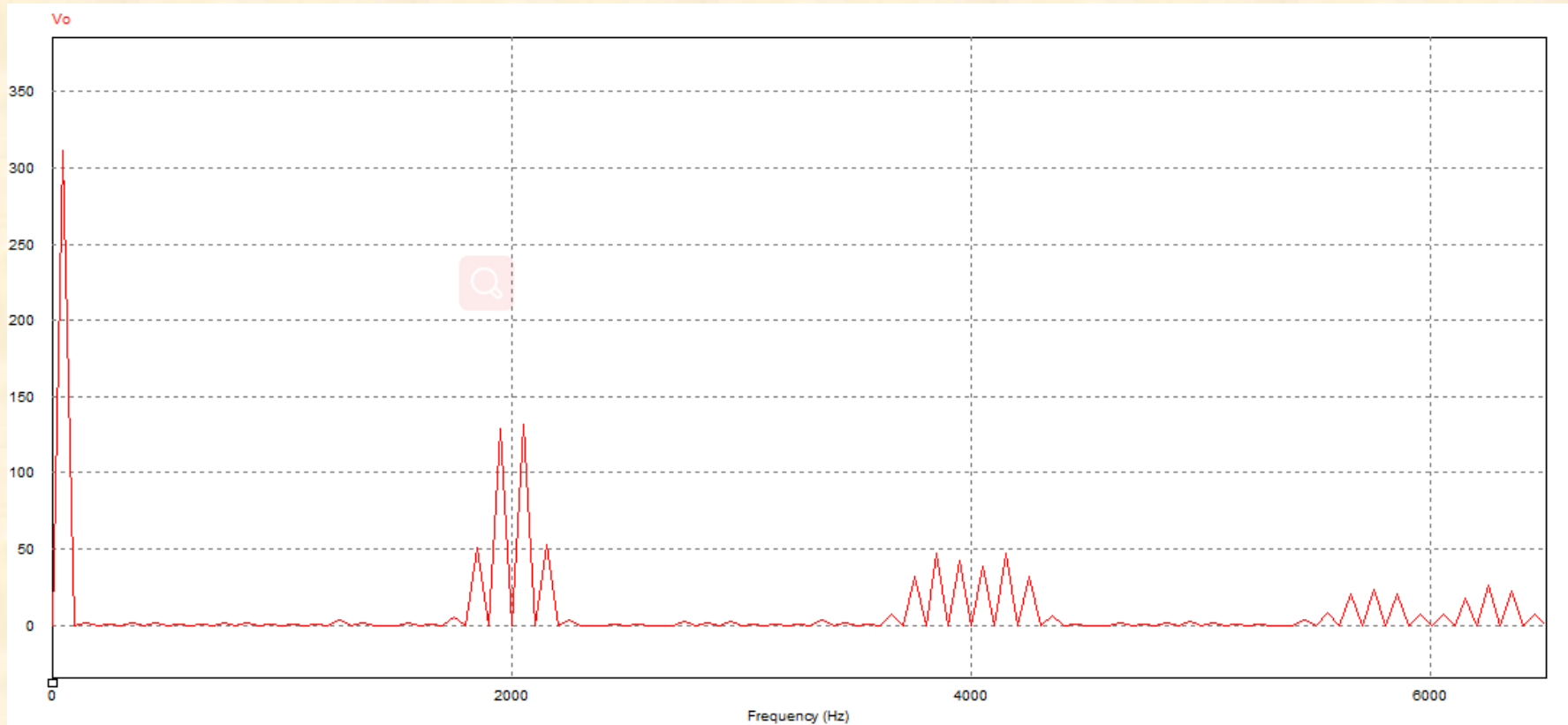

- $U_{o1} = 303V, RMS = \frac{303}{\sqrt{2}} \approx 214.25V$

Unipolar PWM Simulation Results



- Output current I_o

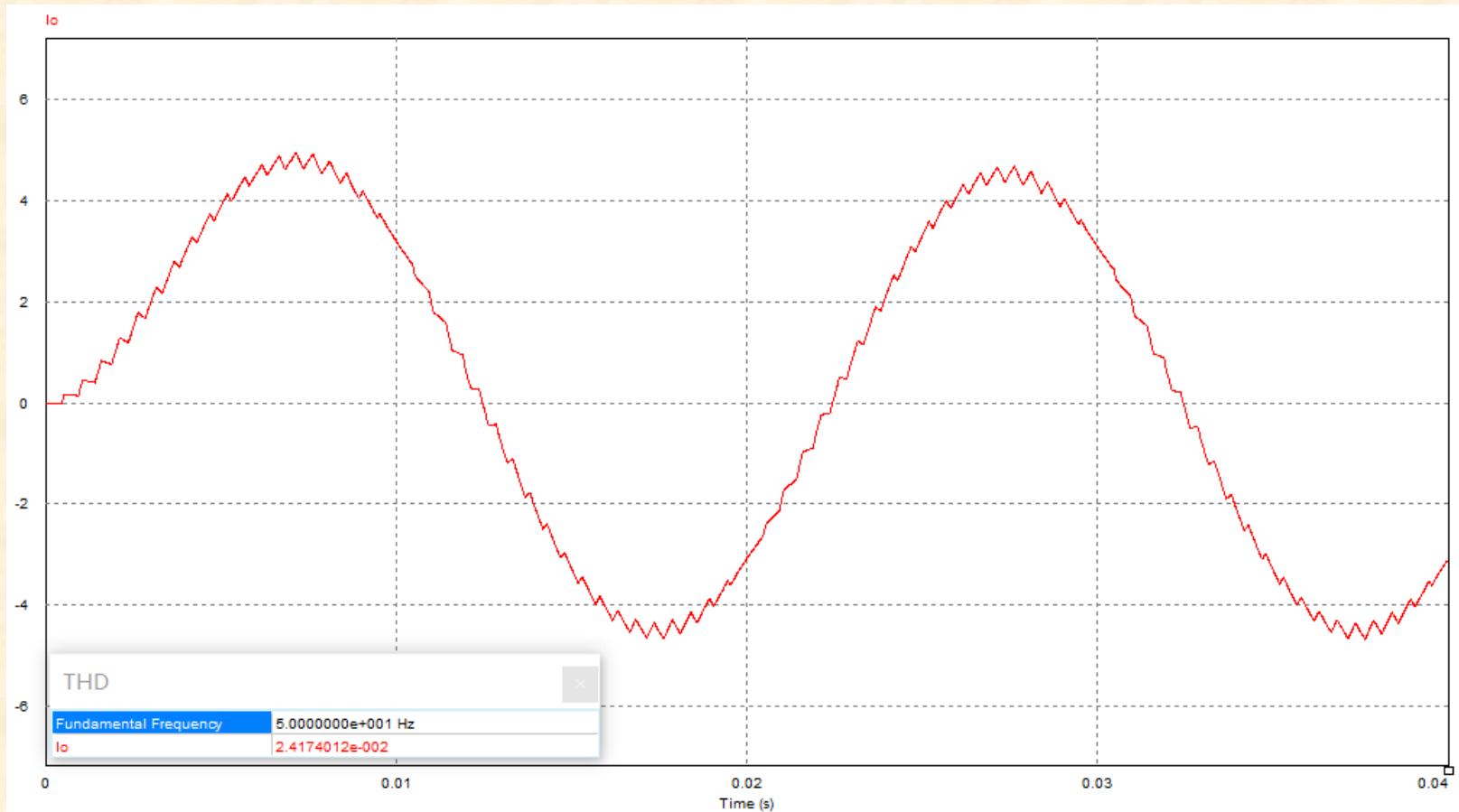

$$THD = 2.42\%$$

Selected Harmonics Elimination PWM

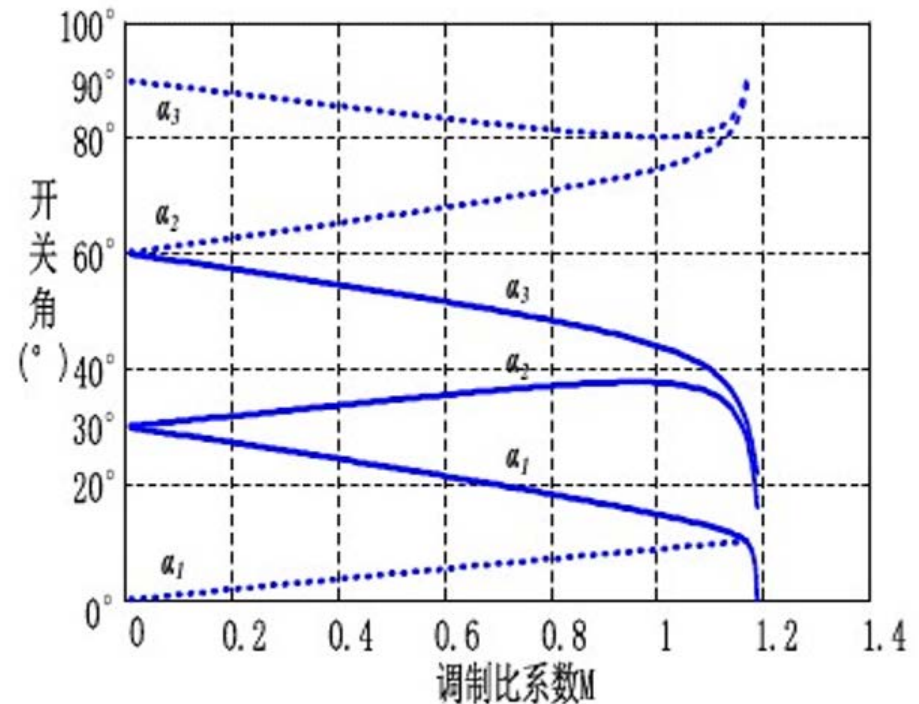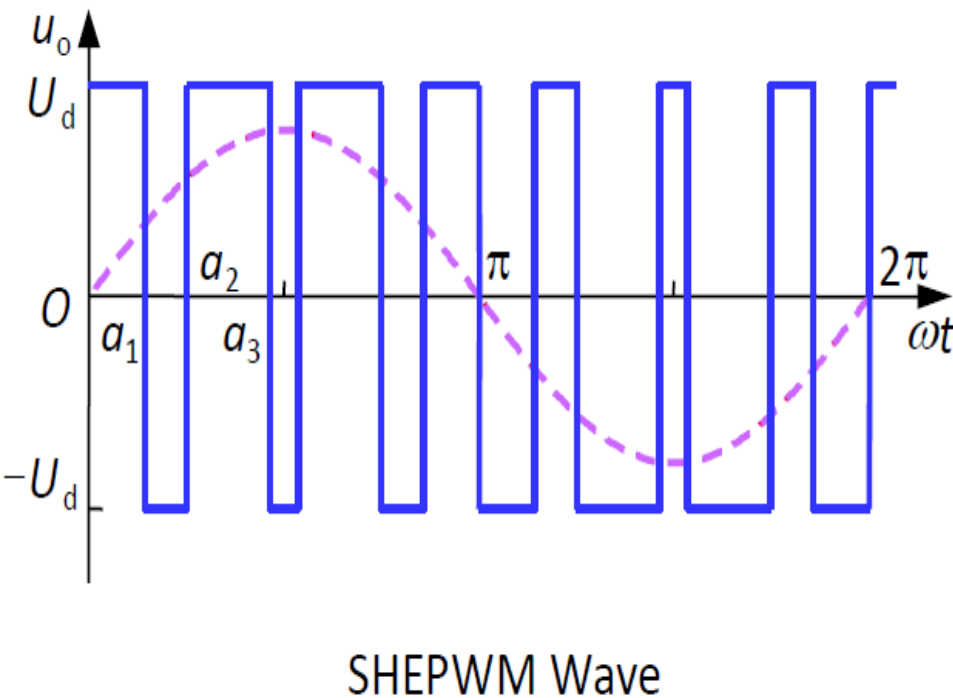
- In a half cycle, each device is turned on or off for three times



- When $m_a = 0.778$, $\alpha_1 = 20^\circ$, $\alpha_2 = 35^\circ$, $\alpha_3 = 50^\circ$.


SHEPWM Modulation Model

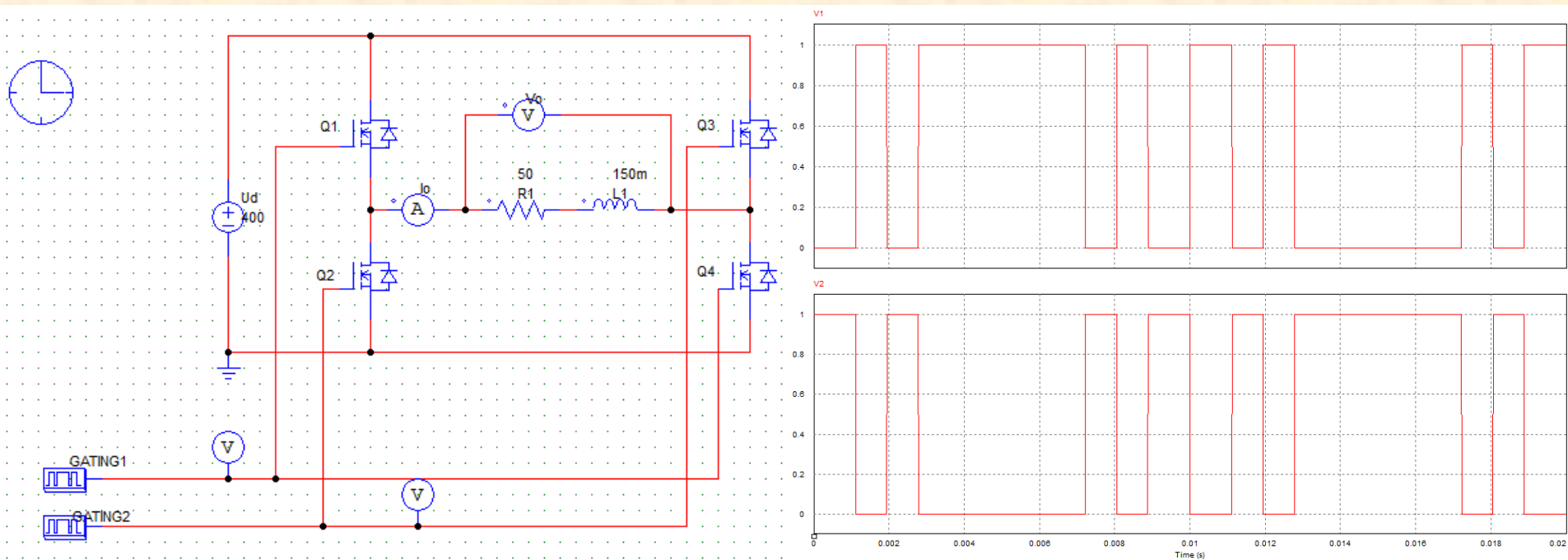- Gating1=1 , Q_1 and Q_4 on, $U_o = U_d$
- Gating2=1 , Q_2 and Q_3 on, $U_o = -U_d$



SHEPWM Simualtion Result

- Output PWM voltage and current

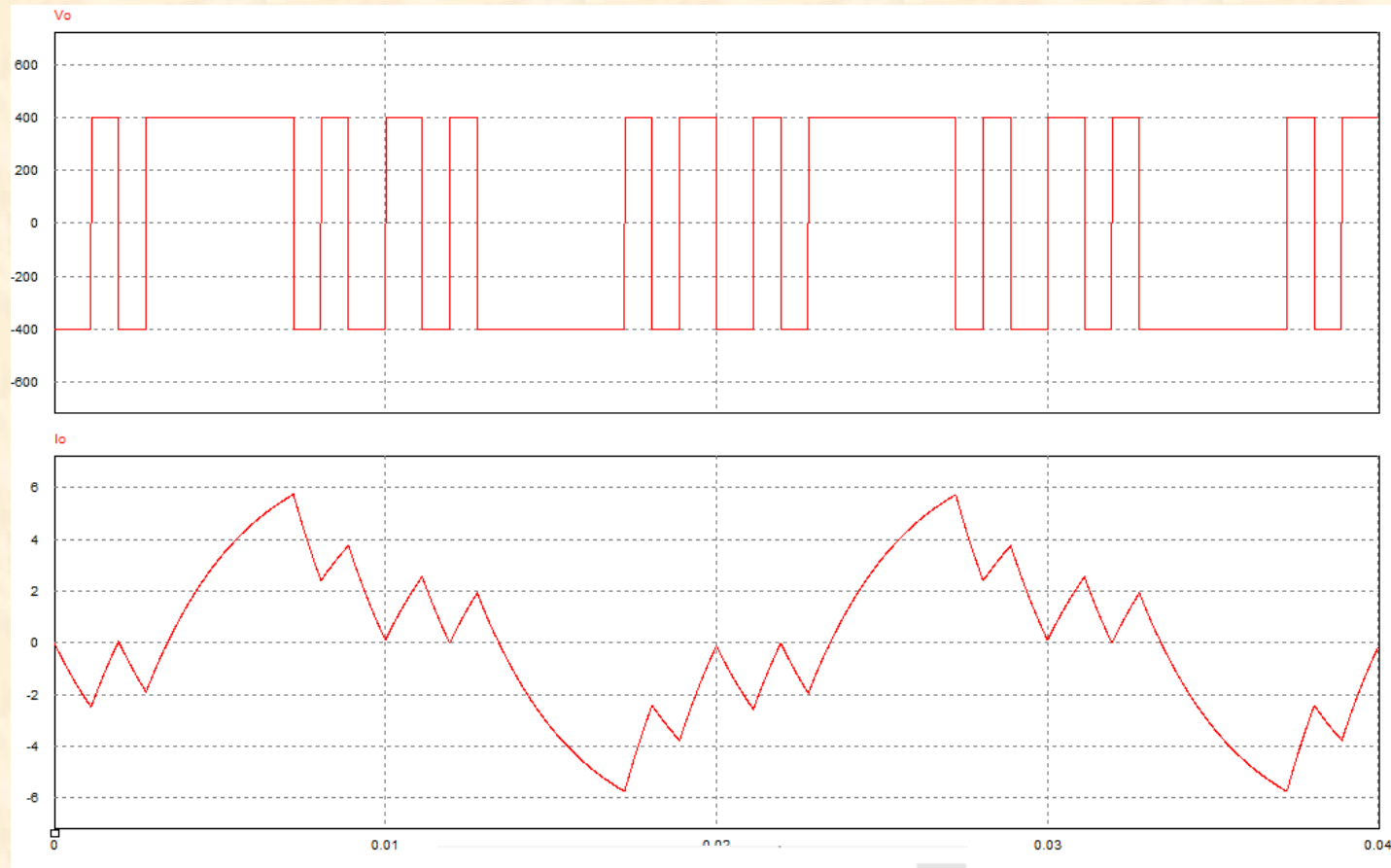


THD	
Fundamental Frequency	5.0000000e+001 Hz
V_o	1.8554689e+000
I_o	4.1355340e-001

SHEPWM Simulation Result

- FFT analysis

	Frequency	Vo
1	50	268.79
3	150	206.38
5	250	5.79
7	350	20.24
9	450	248.29
11	550	292.22
13	650	20.02
15	750	125.42
17	850	23.62

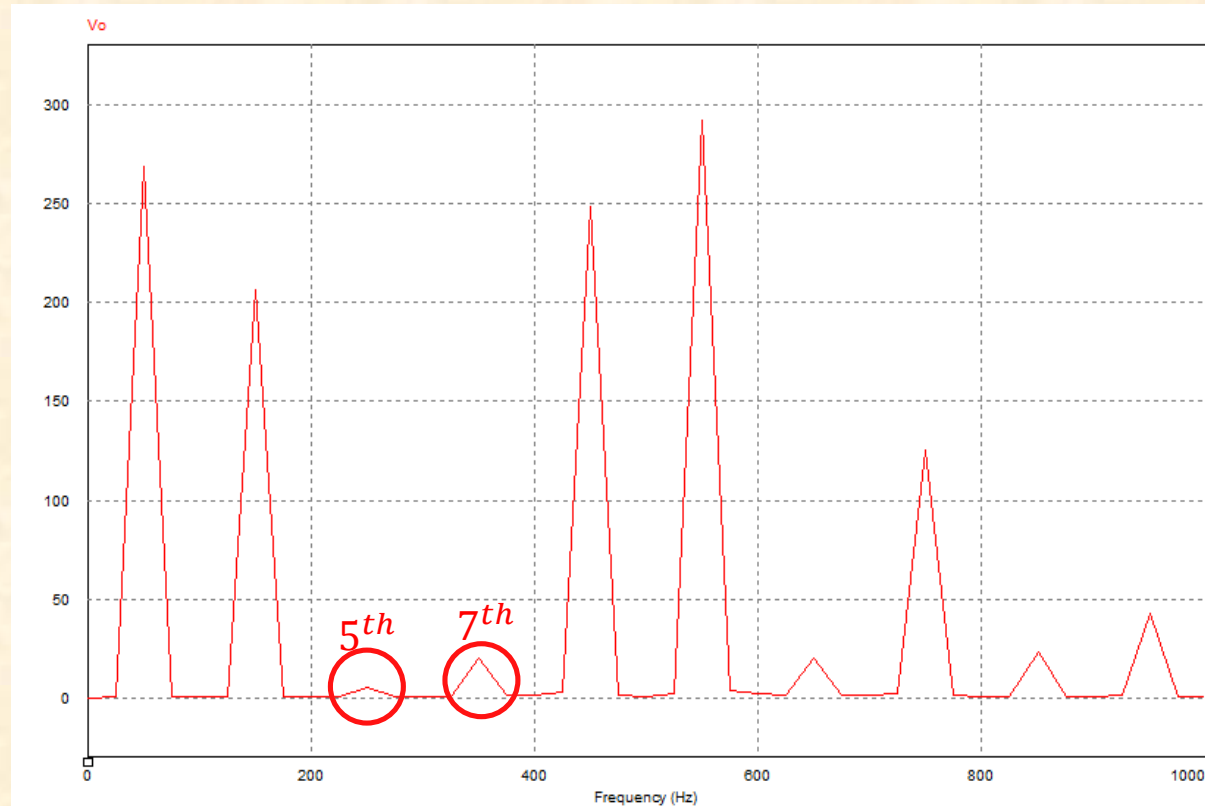

- The 5th and 7th order harmonics of U_o are almost zero. (read the switch angle inaccurately)

Conclusion

- Bipolar PWM :
 - The modulation circuit is easy to implement
- Unipolar PWM :
 - Lower THD
 - Lower amplitude of the minimum order harmonic
- SHE PWM
 - Lower switch frequency
 - Elimination selected harmonics
 - Three-phase can eliminate 3th order harmonics



Thanks for your kind attention!

Jiawei Liang

ShanghaiTech University, July 11th, 2019